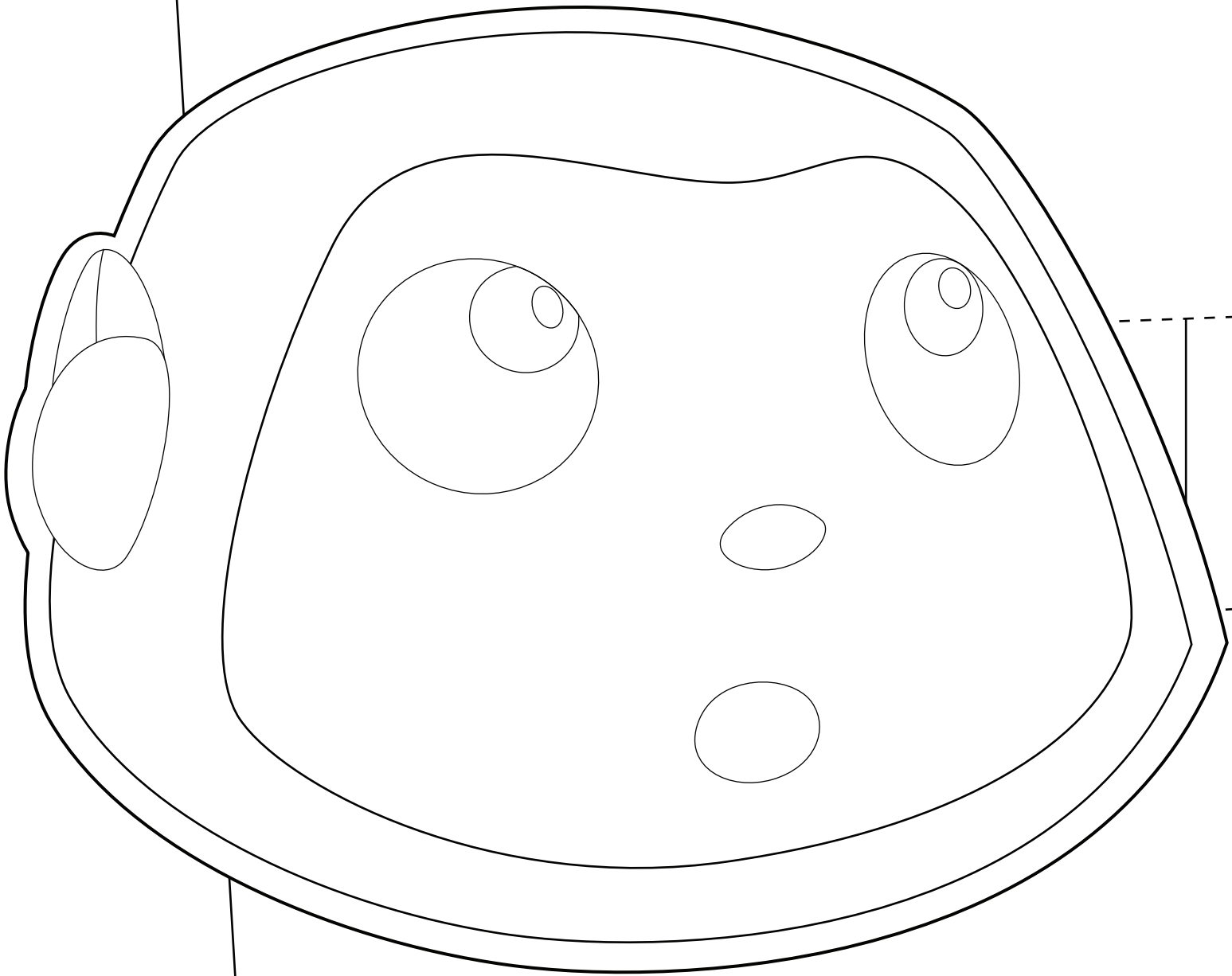


# THE FIRST CHRISTMAS



# STEM ACTIVITY

# WHAT YOU NEED




## AA BATTERY

You'll need one per craft.


## STRING OF LIGHTS

Use LED lights.

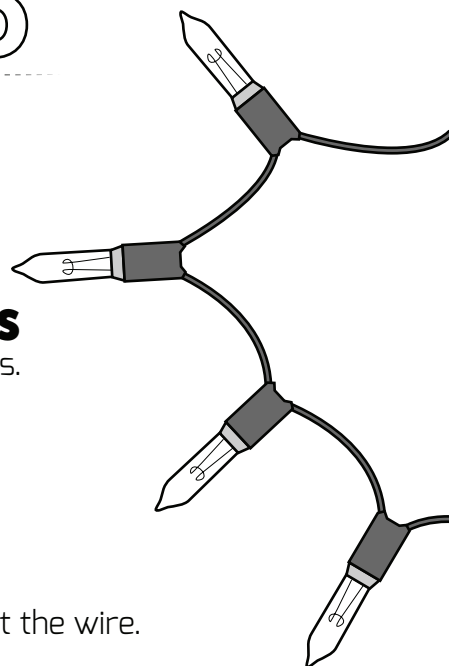

## ELECTRIC TAPE

Regular tape may not hold charge.

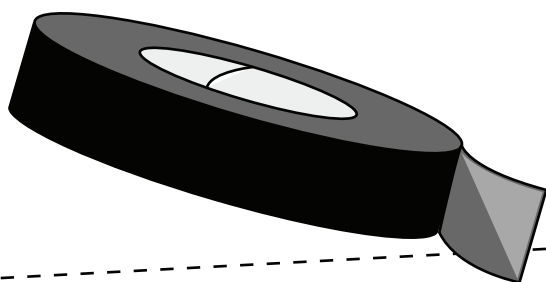

## WIRE CUTTERS


These will be used to cut the wire.

# DIRECTIONS

## STEP 1
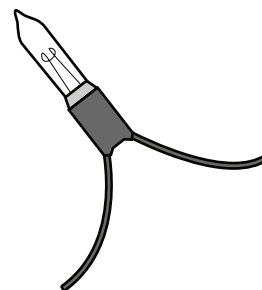
### *Before Class:*


Use wire cutters to cut the string of lights into separate pieces, each containing one bulb.



## STEP 2
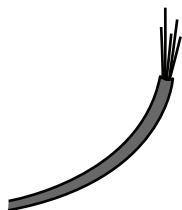
### *Before Class:*

Strip the ends of the wire to create a contact point on each end.



## STEP 3

Use electric tape to secure one end of the wire to the positive end of the AA battery, and one end to the negative side.

## RESULTS

If done correctly, the LED should light up. If it does not light up, make sure that the bulb is working and that the battery is not dead. **Enjoy!**

